

# **EE 611 – 2019 Microwave Integrated Circuits**

## **Course Project**

### **Butler Matrix Design**

#### **1. Problem Statement:**

Design a Broadband 4X4 Butler Matrix Circuit Using Microstrip Transmission line at the frequency of operation 5.4 GHz. The design is to be fabricated on FR – 4 substrate with  $\epsilon_r = 4.4$ ,  $h = 1.6$  mm,  $\tan \delta = 0.02$ .

#### **2. Procedure:**

- a. Design the Butler Matrix using Ideal T-Lines
  - i. Butler Matrix is a combination of  $90^\circ$  Hybrids and phase delay lines.
  - ii. Design a  $90^\circ$  hybrid and verify its function.
  - iii. Then take the proper combination of  $90^\circ$  hybrids and delay lines, design 4X4 Butler Matrix.
- b. Verify the same with the microstrip Transmission line
- c. Generate the corresponding layout
  - i. After verifying the design, Using Generate layout function, generate the layout of the design.
  - ii. Add some M-lines and curved paths, such that no line is overlapped in the layout.
  - iii. Now assign ports to the layout and verify the results
  - iv. If the results are good, then go for fabrication.
- d. Print the layout on Butter paper and give it in the PCB lab for fabrication.